

ELEC3607 Embedded Systems

A Simple SDR


Philip Leong (philip.leong@sydney.edu.au)







School of Electrical and Information Engineering



THE UNIVERSITY OF
SYDNEY

- › A software-defined radio (SDR) is a radio where components that have been traditionally implemented in analogue hardware (e.g. mixers, filters, amplifiers, modulators/demodulators, detectors, etc.) are instead implemented in software
 - › In ELEC3607 we are going to construct an SDR receiver (signal of interest is 7.0386 MHz, 200 Hz bandwidth)
 - › The SDR is designed for simplicity rather than performance
 - A high-performance design would have more filtering, more attention to power supply rejection, etc
 - Circuit comes from <https://circuitsalad.com/2020/11/13/>
 - › Note an understanding of the signal processing theory and the electronics are needed to make any system (we focus on the embedded systems aspects)
 - An excellent tutorial on quadrature signals is here <https://www.dsprelated.com/showarticle/192.php>
-

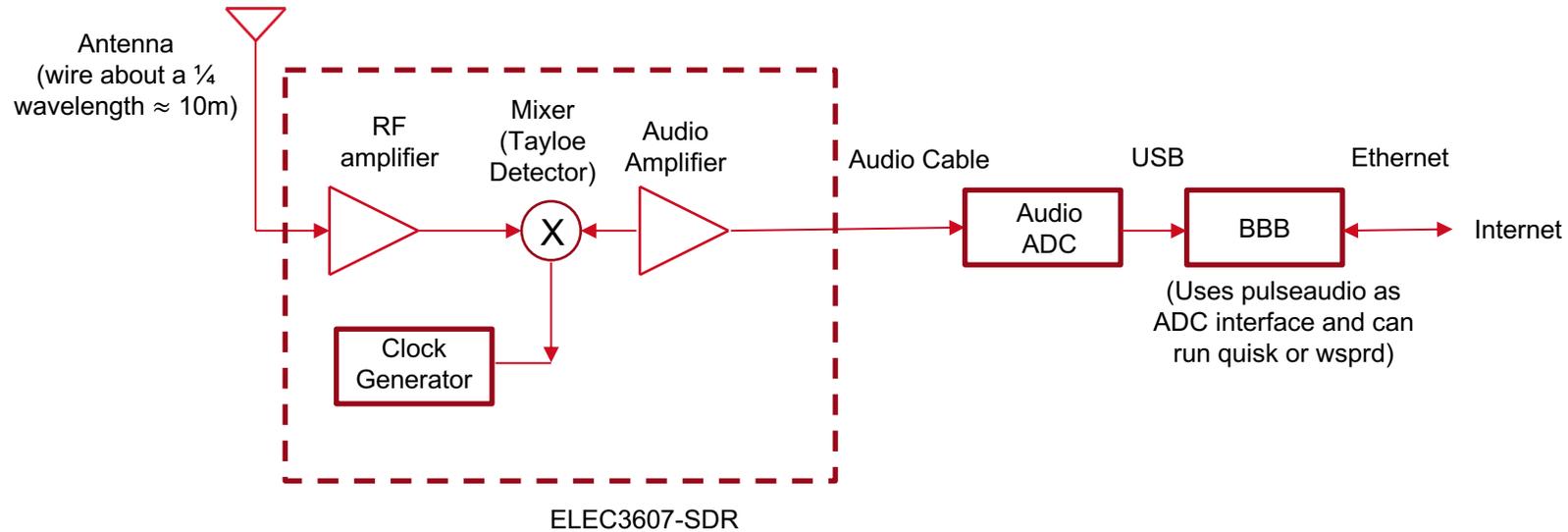

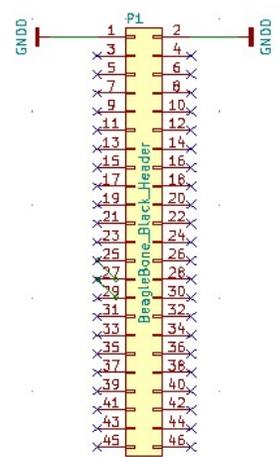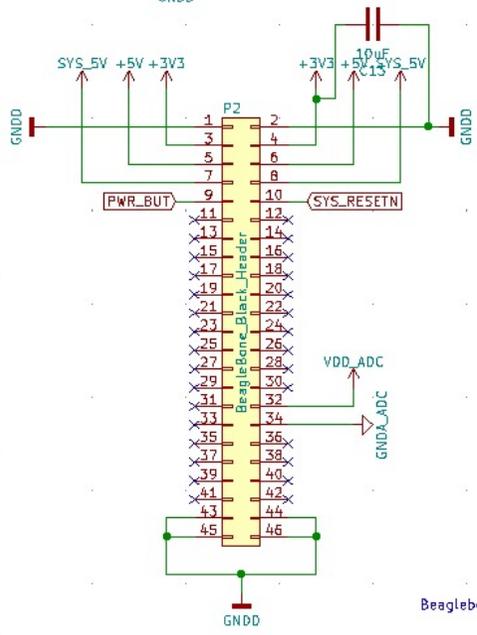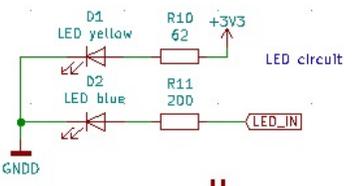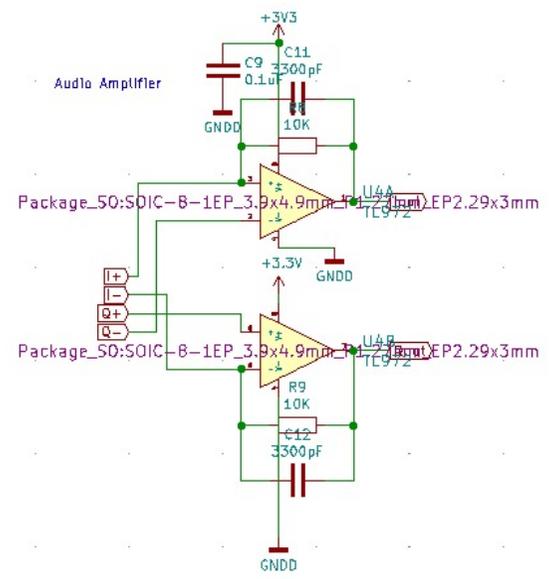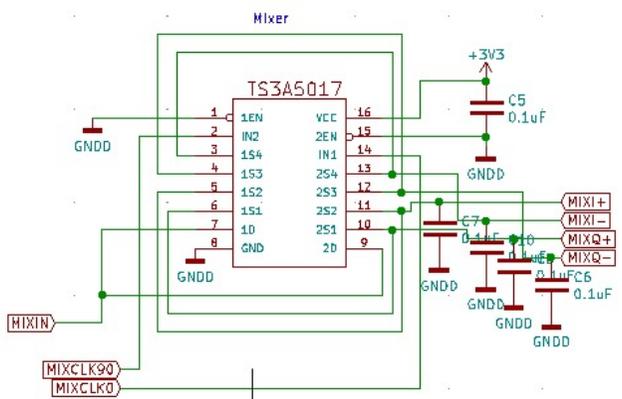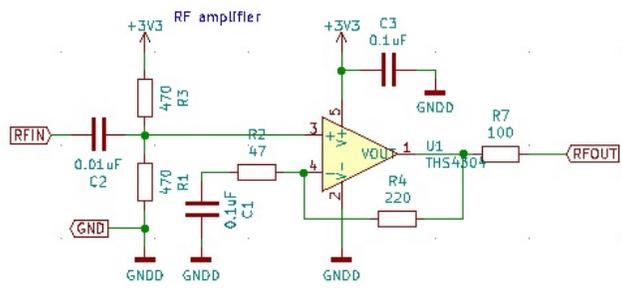


From: <https://circuitsalad.com/2020/11/13/the-fv-1-based-sdr-revisited/>

Sheet: 1/1
File: bbb.sch

Title: ELEC3607 Software Defined Radio

Size: A4	Date: 4/2/2021	Rev: 0.1
KiCad E.D.A. kicad (5.1.9-0-10_14)		Id: 1/1

Mandatory to have LEDs!

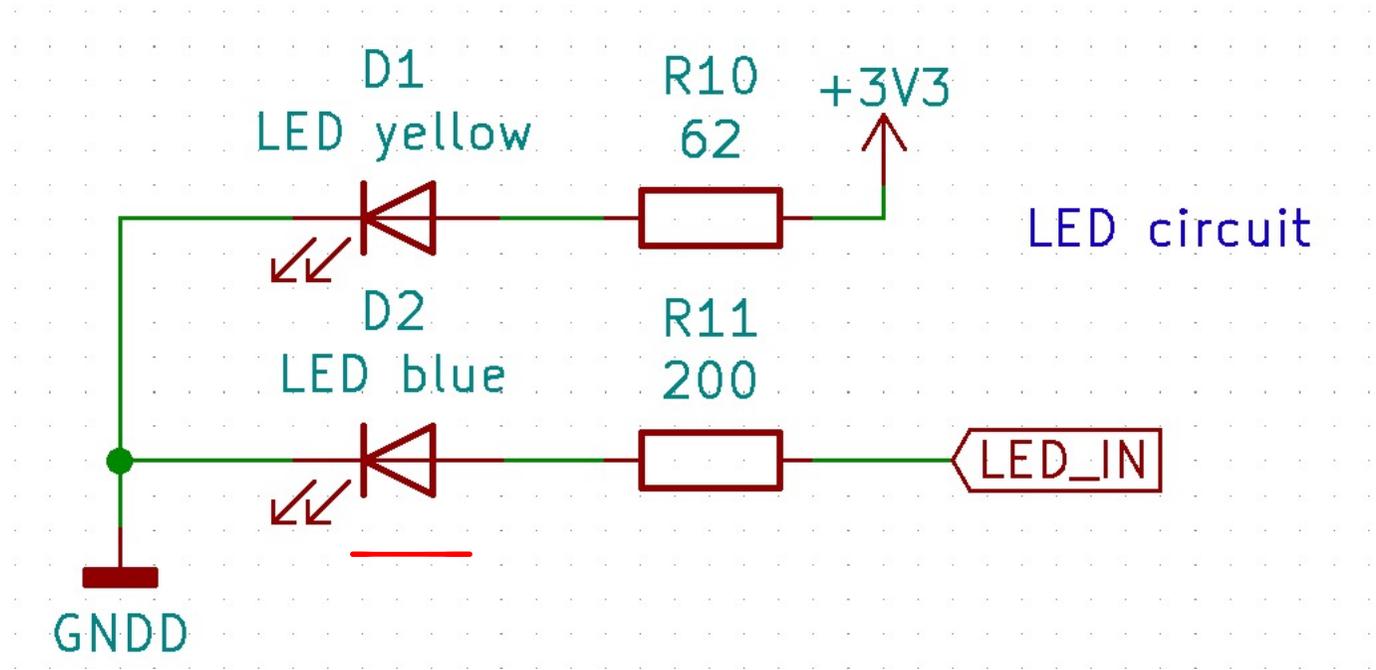

Simple non-inverting amplifier <https://www.ti.com/lit/an/sboa224a/sboa224a.pdf>


Not a great design (see <https://www.analog.com/en/analog-dialogue/articles/avoiding-op-amp-instability-problems.html>)

Datasheet: <https://www.ti.com/product/THS4304> (low noise, rail-to-rail, high GBW)

High freq gain $G=1+R4/R2$, low freq gain=1 due to C1

C2 AC couples the input, R1 and R3 make DC level of $V+ 3.3V/2$

C3 is to bypass the 3.3V supply

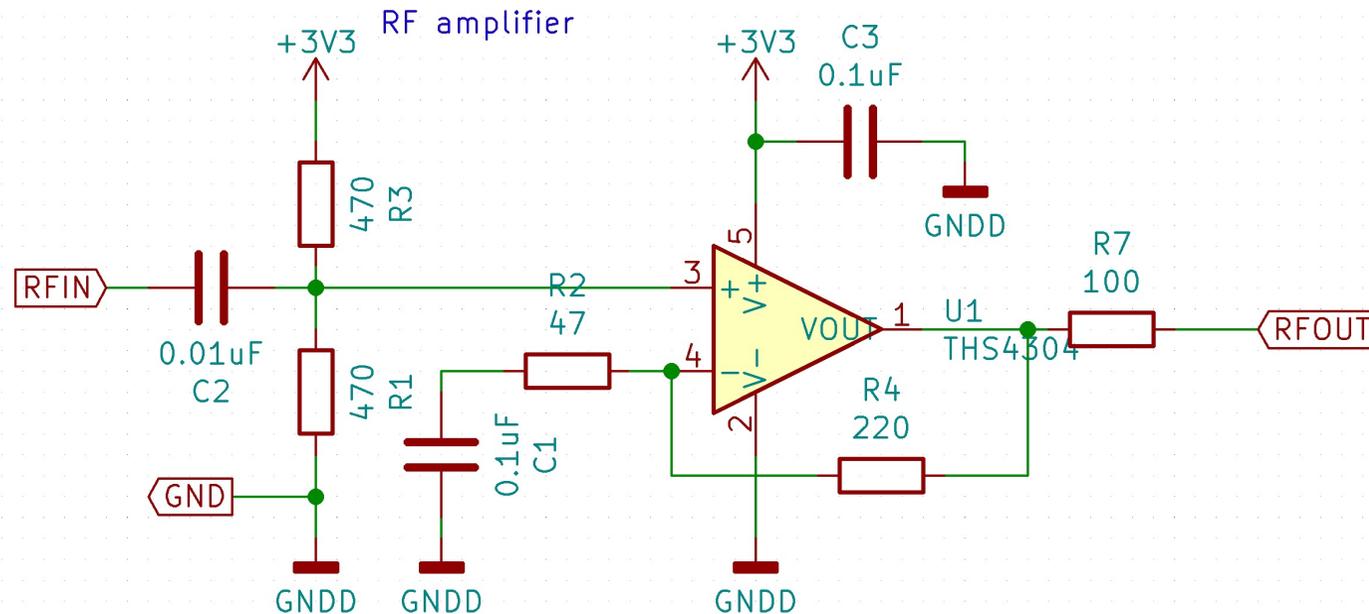


<https://www.silabs.com/timing/clock-generators/cmos/device.si5351a-b-gt>

Will program this via BGG to produce two square wave signals CLK0 and CLK1 at appropriate frequency with 90° phase difference

Interface is i2c (discussed later)

C4 is to bypass the 3.3V supply


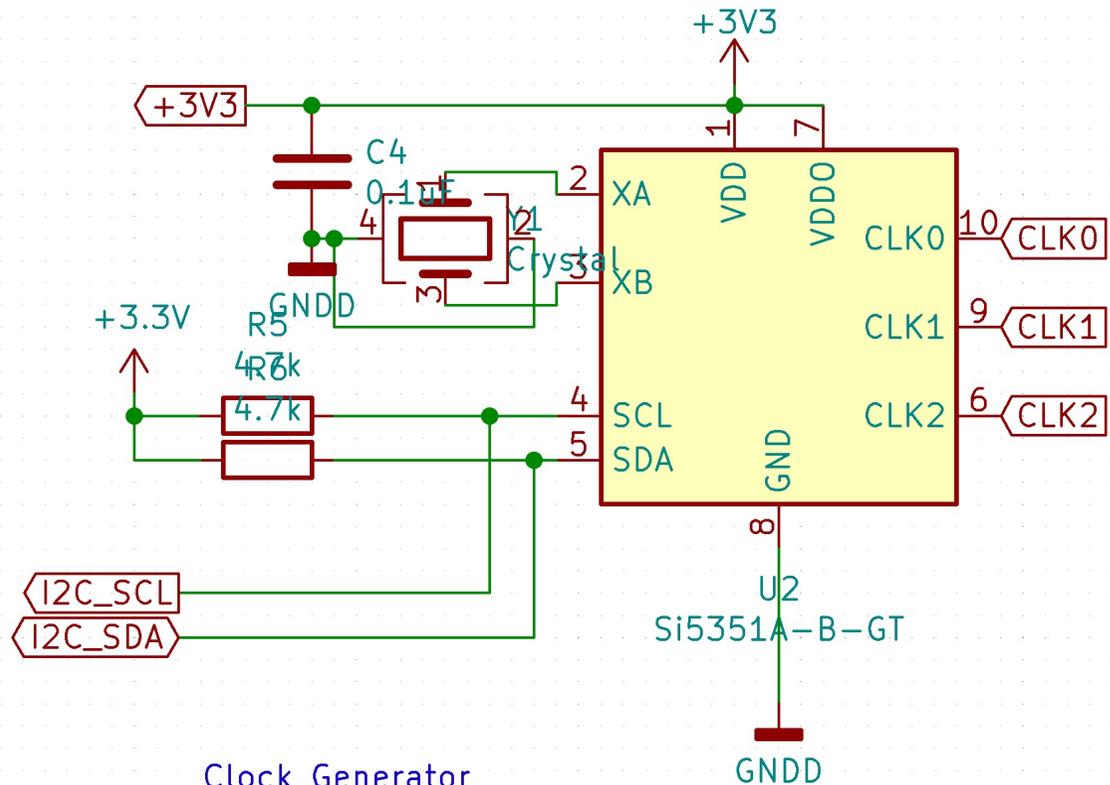


Clock Generator

This is a Taylor detector (http://www.norcalqrp.org/files/Taylor_mixer_x3a.pdf)

Datasheet <https://www.ti.com/lit/ds/symlink/ts3a5017.pdf?ts=1614679120382>



C5 is to bypass the 3.3V supply

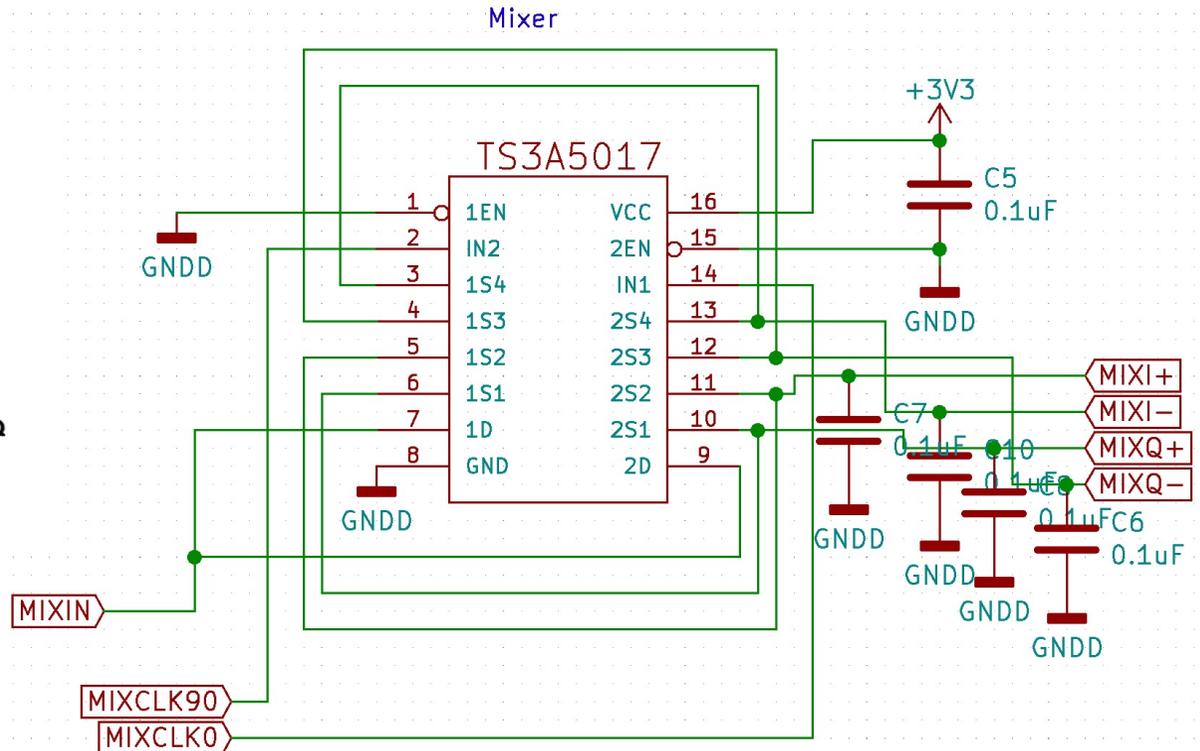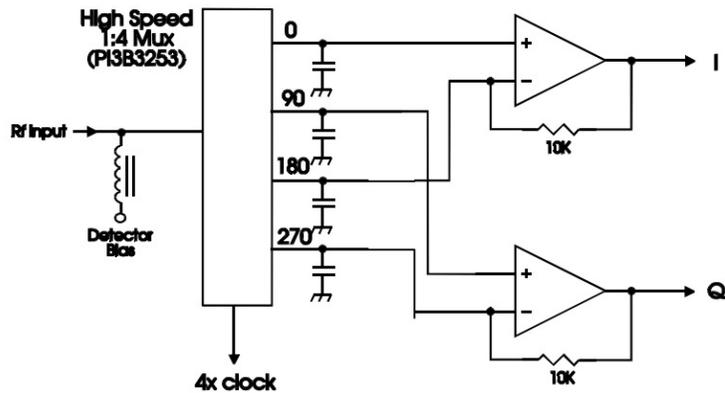

This is an integrator circuit <https://www.ti.com/lit/an/sboa275a/sboa275a.pdf>

Datasheet <https://www.ti.com/product/TL972>

C9 is to bypass the 3.3V supply

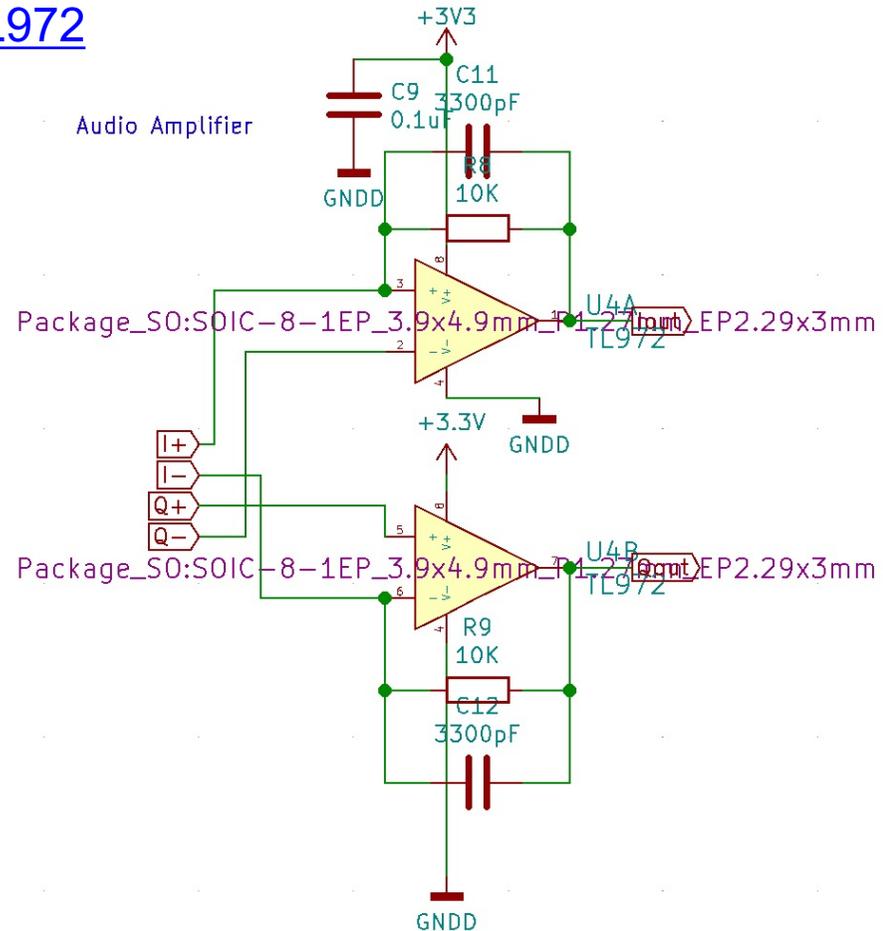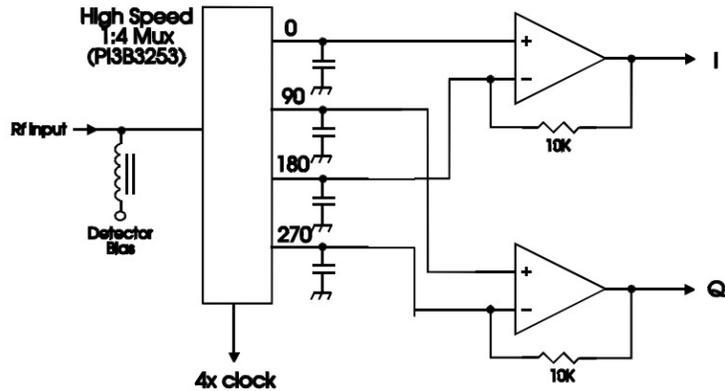

All blocks described are connected to this connector

The BBG will be used to program the Clock Generator and to further process the I/Q output

